



# VLSI DESIGN AND TESTING (BEC602)

Padmavathi N

Associate Professor

Department of ECE

# Course objectives

1. This course deals with analysis and design of digital CMOS integrated circuits.
2. The course emphasizes on basic theory of digital circuits, design principles and techniques for digital design blocks implemented in CMOS technology.
3. This course will also cover switching characteristics of digital circuits along with delay and power estimation.
4. Understanding the CMOS sequential circuits and memory design concepts.
5. Explore the knowledge of VLSI Design flow and Testing

# Course Outcomes (COs)

- After completing the course, the students will be able to

**CO1** -Apply the fundamentals of semiconductor physics in MOS transistors and analyze the geometrical effects of MOS transistors

**CO2**- Design and realize combinational, sequential digital circuits and memory cells in CMOS logic.

**CO3**- Analyze the synchronous timing metrics for sequential designs and structured design basics.

**CO4**- Understand designing digital blocks with design constraints such as propagation delay and dynamic power dissipation.

**CO5** -Understand the concepts of Sequential circuits design and VLSI testing

# Text Books

- 1. Principals of CMOS VLSI Design A System approach Neil H E Weste and Kamran Eshraghain . Addition Wisley Publishing company.
- 2. “CMOS Digital Integrated Circuits: Analysis and Design”, Sung Mo Kang & Yosuf Leblebici, Third Edition, Tata McGraw-Hill.

# Module 1 Syllabus

- **Introduction to CMOS Circuits:** Introduction, MOS Transistors, MOS Transistor switches, CMOS Logic, Alternate Circuit representation, CMOS-nMOS comparison.
- [Text 1: 1.1,1.2,1.3,1.4,1.5.1.6.]

# Module 2 Syllabus

- **MOS Transistor Theory:** n-MOS enhancement transistor, p-MOS transistor, Threshold Voltage,
- Threshold voltage adjustment, Body effect, MOS device design equations, V-I characteristics, CMOS
- inverter DC characteristics, Influence of  $\beta_n / \beta_p$  ratio on transfer characteristics, Noise margin,
- Alternate CMOS inverters. Transmission gate DC characteristics. Latch-up in CMOS.
- [Text 1: 2.1,2.2,2.3,2.4,2.5.2.6.]

# Module3 Syllabus

- **MOS Transistor Theory:** n-MOS enhancement transistor, p-MOS transistor, Threshold Voltage,
- Threshold voltage adjustment, Body effect, MOS device design equations, V-I characteristics, CMOS
- inverter DC characteristics, Influence of  $\beta_n / \beta_p$  ratio on transfer characteristics, Noise margin,
- Alternate CMOS inverters. Transmission gate DC characteristics. Latch-up in CMOS.
- [Text 1: 2.1,2.2,2.3,2.4,2.5.2.6.]

# Module 4 Syllabus

- **CMOS Circuit and Logic Design:** Introduction, CMOS Logic structures, CMOS Complementary logic,
- Pseudo n-MOS logic, Dynamic CMOS logic, Clocked CMOS Logic, Cascade Voltage Switch logic, Pass transistor Logic, Electrical and Physical design of Logic gates, The inverter, NAND and NOR gates, Body effect, Physical Layout of Logic gates, Input output Pads.
- [Text 1: 5.1,5.2,5.2.1, , 5.2.2, 5.2.3, 5.2.4, 5.2.6, 5.2.8, 5.3,5.3.1,5.3.2, 5.3.4 ,5.3.8,5.5]



# Module 5 Syllabus

- **Sequential MOS Logic Circuits:** Introduction, Behaviour of Bistable Elements (Excluding
- Mathematical analysis) SR Latch Circuit, Clocked Latch and Flip-Flop Circuits, Clocked SR Latch,
- Clocked JK Latch.
- [Text2: 8.1, 8.2, 8.3, 8.4]
- **Structured Design and Testing:** Introduction, Design Styles, Testing
- [Text1: 6.1, 6.2. 6.5]

# ***Contents***

- ***What is VLSI ?***
- ***An Preview.***
- ***VLSI World.***
- ***Moore Law.***
- ***VLSI Industry.***
- ***Objective for VLSI Design.***
- ***Applications.***
- ***Future of VLSI.***

# Identify the Image



*5 MB Hard Drive being Shipped by IBM - 1956.*

# ***This is Called VLSI Advancement !***




5MB (IBM)-1956, Cost - \$10,000/ 1 MB




4TB (WB)-2013

***This achieved because of VLSI***

 

***Charles Babbage designed the first computer, starting in 1823***

## *Unbelievable facts*

 

*AVIDAC was the first digital computer at Argonne National Laboratory, and began operating in 1953. It was built by the Physics Division for \$250,000. Pictured shown AVIDAC, is pioneer Argonne computer scientist Jean F. Hall. AVIDAC stands for "Argonne Version of the Institute's Digital Automatic Computer" and was based on architecture developed by mathematician John von Neumann.*

# *Apple Development*



Apple I-1976



Apple- 2011

# VLSI


- **Very Large Scale Integration (within IC)**
- How large is Very Large?
  - ✓ SSI (small scale integration)
    - ✓ 7400 series, 10-100 transistors
  - ✓ MSI (medium scale)
    - ✓ 74000 series 100-1000
  - ✓ LSI 1,000-10,000 transistors
  - ✓ **VLSI > 10,000 transistors**
  - ✓ ULSI/SLSI (Not so popular)



# Moore's Law - 2005

Every 18 months, the numbers of transistor is doubles


Transistors  
Per Die

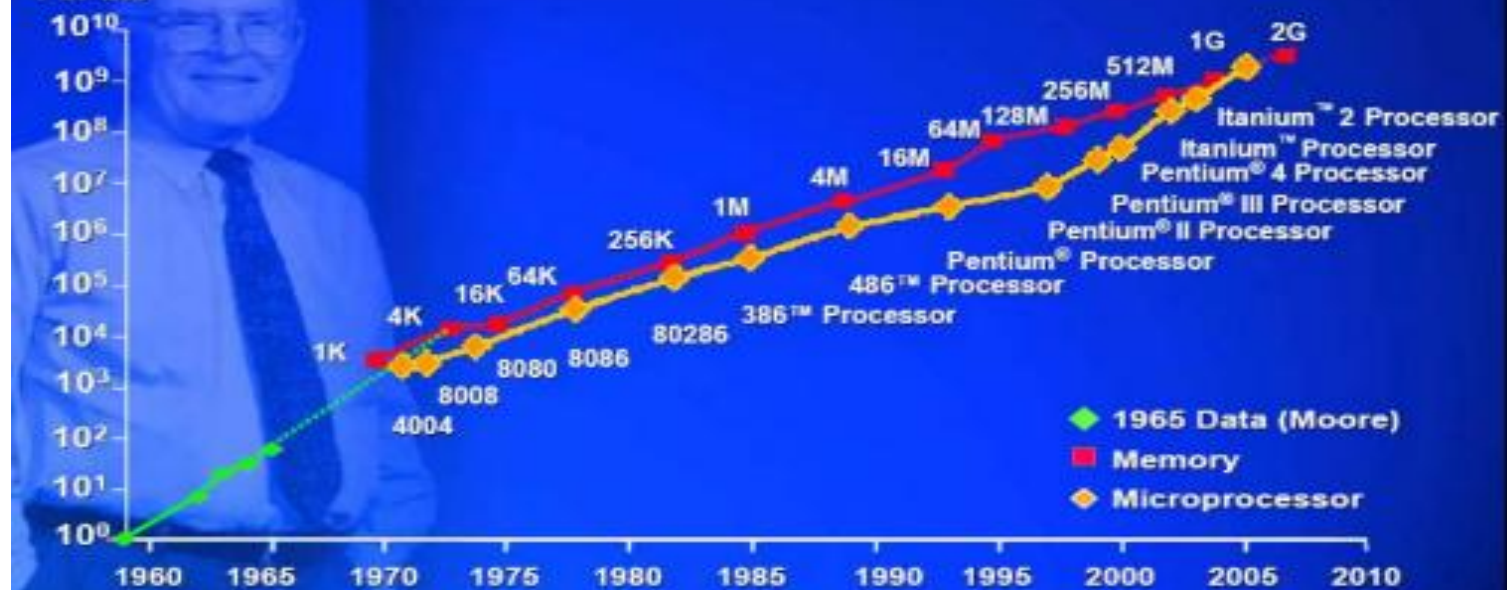

- ◆ 1965 Data (Moore)
- Memory
- ◇ Microprocessor

Source: Intel

# Timeline

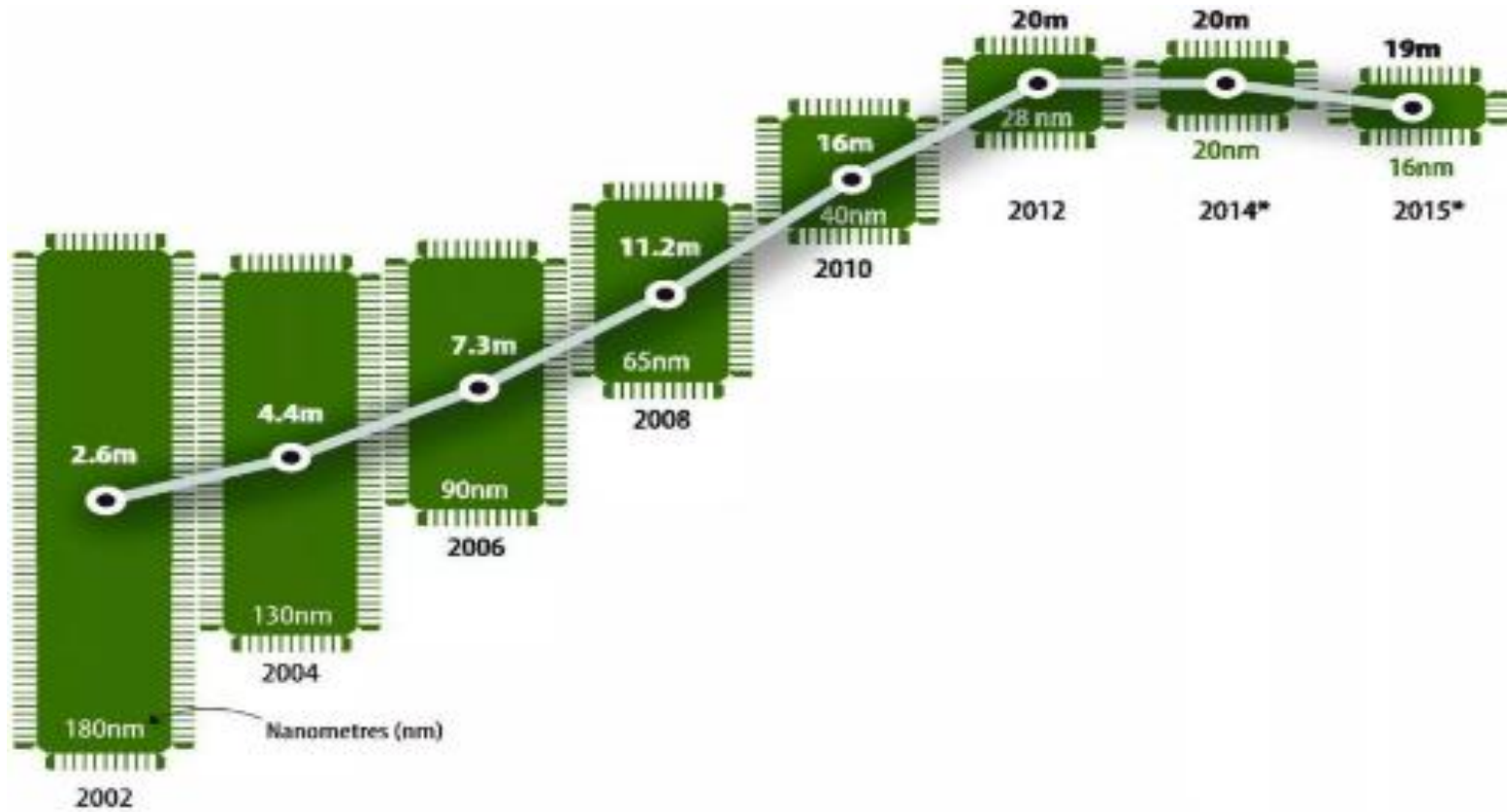


# *Timeline of Electronic Devices*




**Now a Days 2000-2016>> Sensor, Transducer integrated on SOC's**

*Entered to Nanotechnology*

# Power and Size

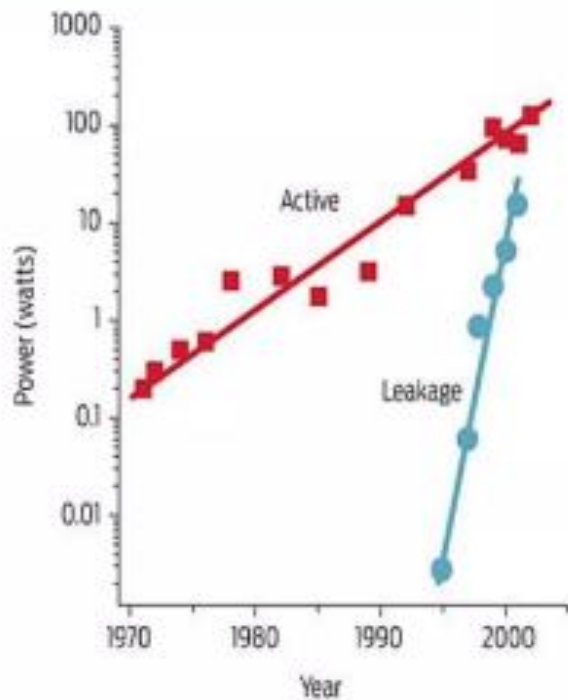

Source: Gordon Moore, Intel; IEEE

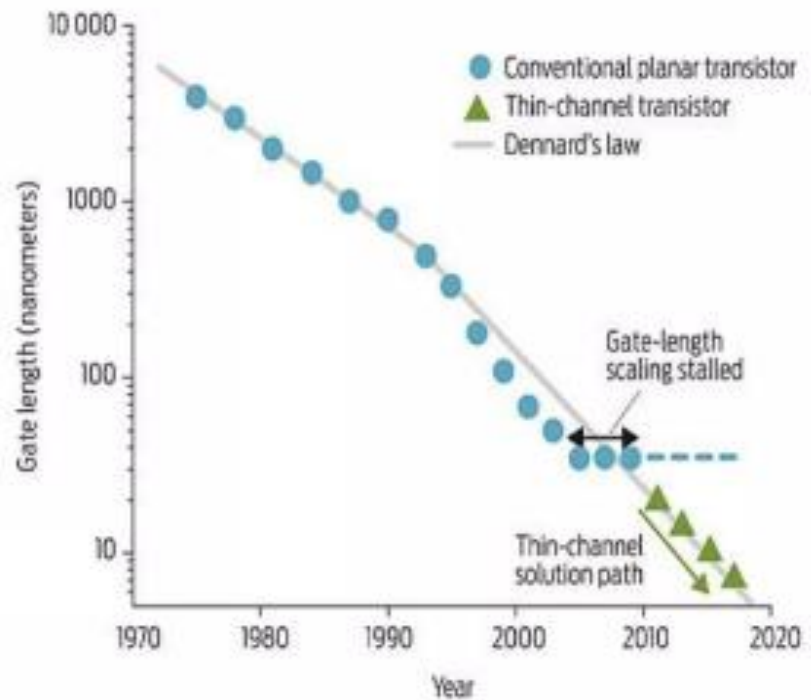

Source: Intel; Khaled Ahmed, Applied Materials

## Sizes of VLSI Chip

- *In 20nm transistors, you can fit around 250 billion of them on a silicon wafer around the size of a fingernail.*



- iPad Air 2 has a custom tri-core ARM CPU and custom octa-core PowerFX GPU, for a total of 3 billion transistors on-die.

# VLSI Companies In India

## VLSI COMPANIES IN INDIA

- [Analog Devices India Product Development Center](#) – Designs DSPs in Bangalore
- [Bit Mapper](#) – Design, development & training
- [CG-CoreEl Programmable Solutions](#) – Design services in telecommunications, networking and DSP
- [Calorex Institute of Technology](#) – Courses in VLSI chip design, DSP and Verilog HDL
- [ControlNet India](#) – VLSI design, network monitoring products and services
- [Cypress Semiconductor](#) – US semiconductor major Cypress has set up a VLSI development center in Bangalore
- [Delsoft](#) – Electronic design automation, digital video technology and VLSI design services
- [E.Infochips](#) – ASIC chip design, embedded systems and software development
- [EDAIndia](#) – Resource on VLSI design centres and tutorials
- [Horizon Semiconductors](#) – ASIC, VLSI and IC design training
- [Microchip Technology](#) – Offers VLSI CMOS semiconductor components for embedded systems
- [Motorola India](#) – IC design center
- [Sandeepani](#) – VLSI design training courses
- [Sanyo LSI Technology](#) – Semiconductor design centre of Sanyo Electronics
- [Semiconductor Complex](#) – Manufacturer of microelectronics equipment like VLSIs & VLSI based systems & sub systems

# CMOS LOGIC

- **What is CMOS?**
  - Complementary Metal-Oxide-Semiconductor logic.
  - Uses both NMOS and PMOS transistors to implement logic functions.
- **Advantages of CMOS Logic:**
  - Low power consumption (no current flow when stable state).
  - High noise immunity.
  - Scalability and integration (large-scale integration, LSI).
- **Basic Logic Gates in CMOS:**
  - NOT, AND, OR, NAND, NOR, XOR, XNOR.

# MOS Transistors-NMOS and PMOS


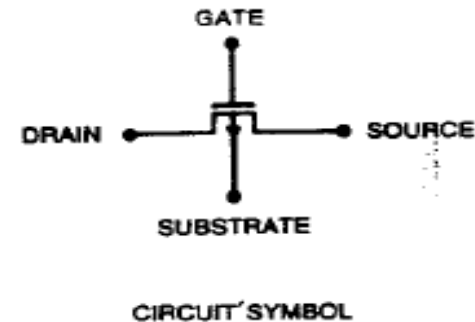
 
 


FIGURE 1.1. MOS transistor physical structures

 

# MOS Transistor switches


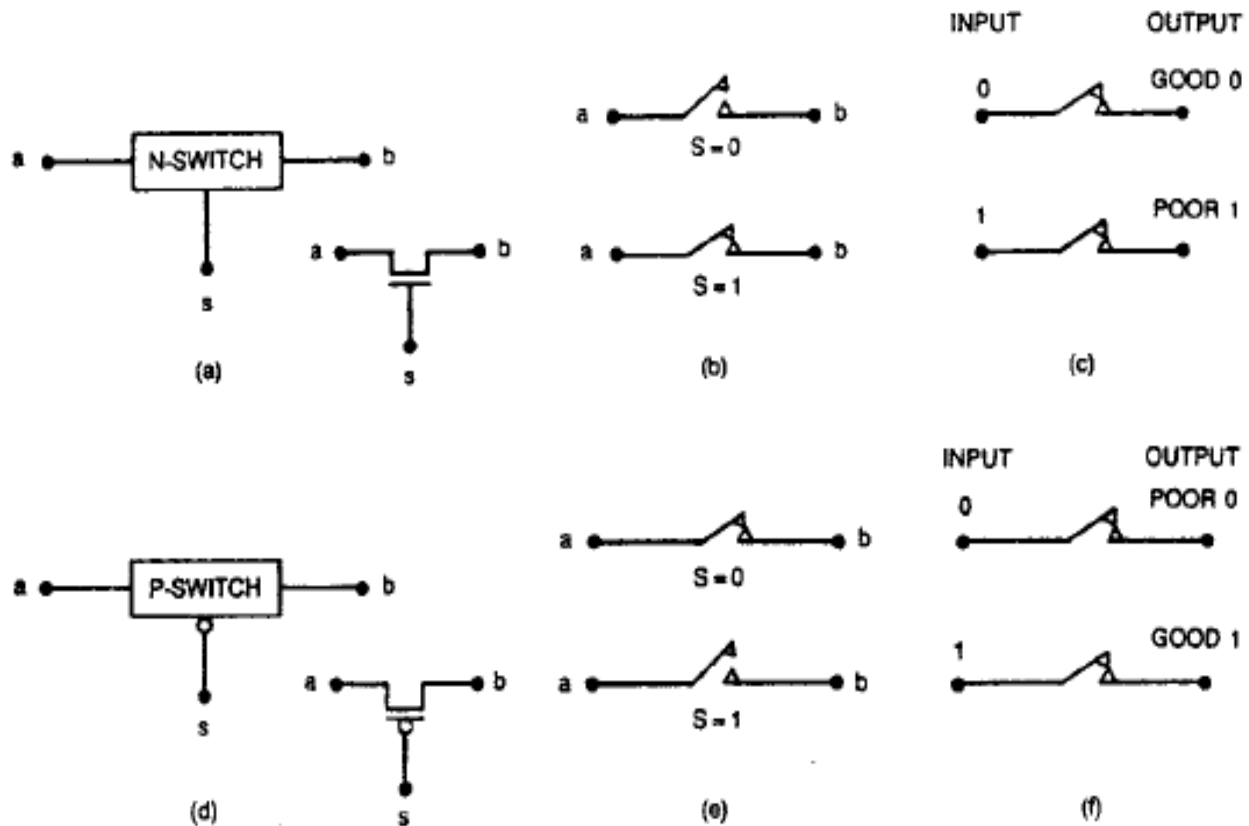
 
 
 


FIGURE 1.2. MOS transistors viewed as switches

# Complementary Switch-C switch


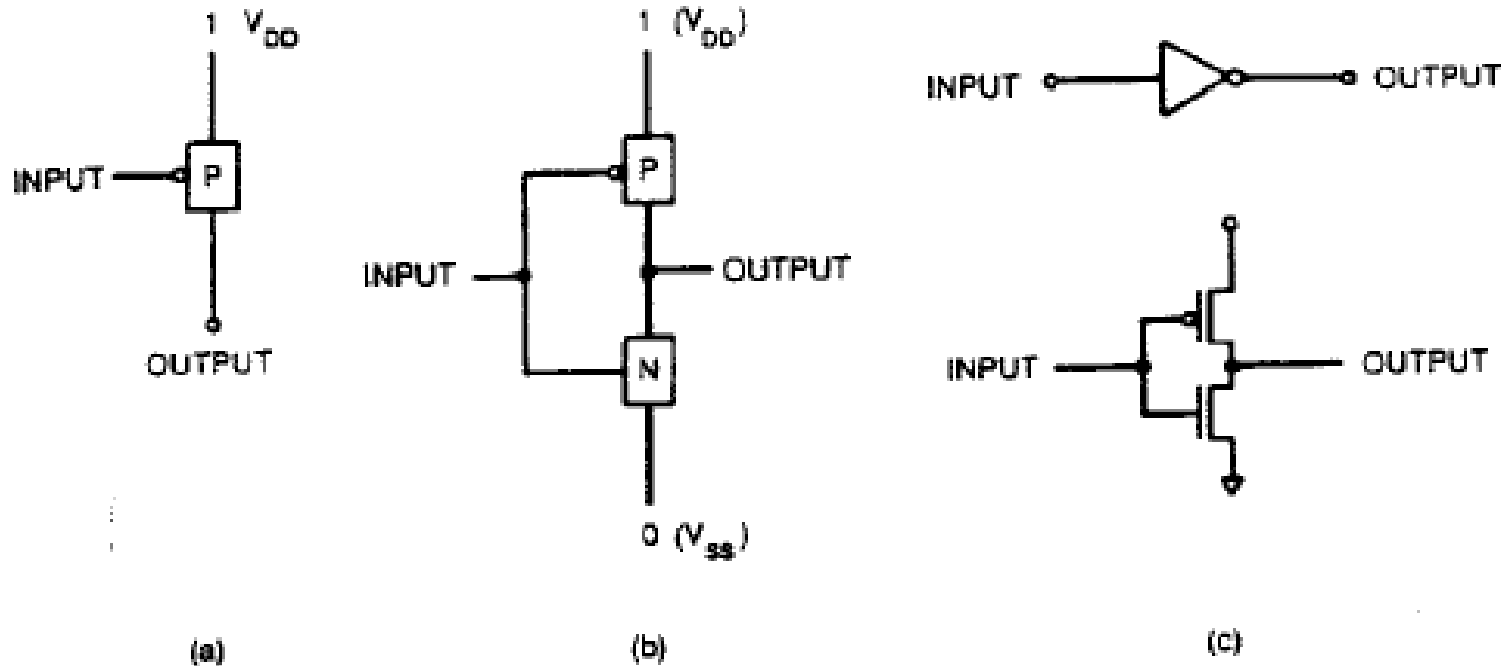

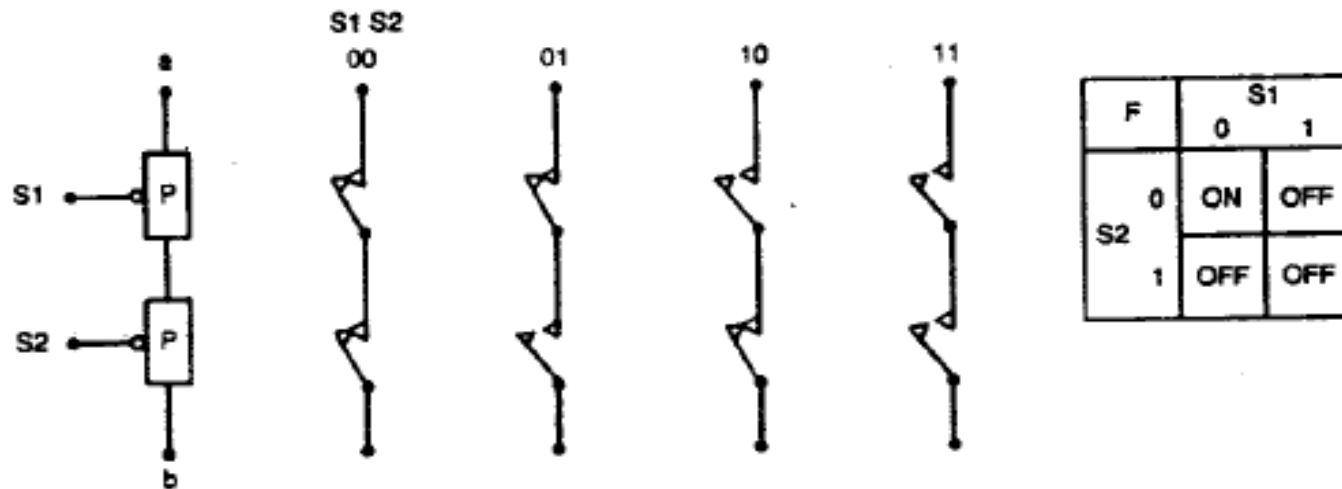 
# CMOS Logic-Inverter


 


**FIGURE 1.4.** Construction of a CMOS inverter

# Combinational Logic-Series switches

 

# Combinational Logic-Parallel switches



# CMOS NAND Gate

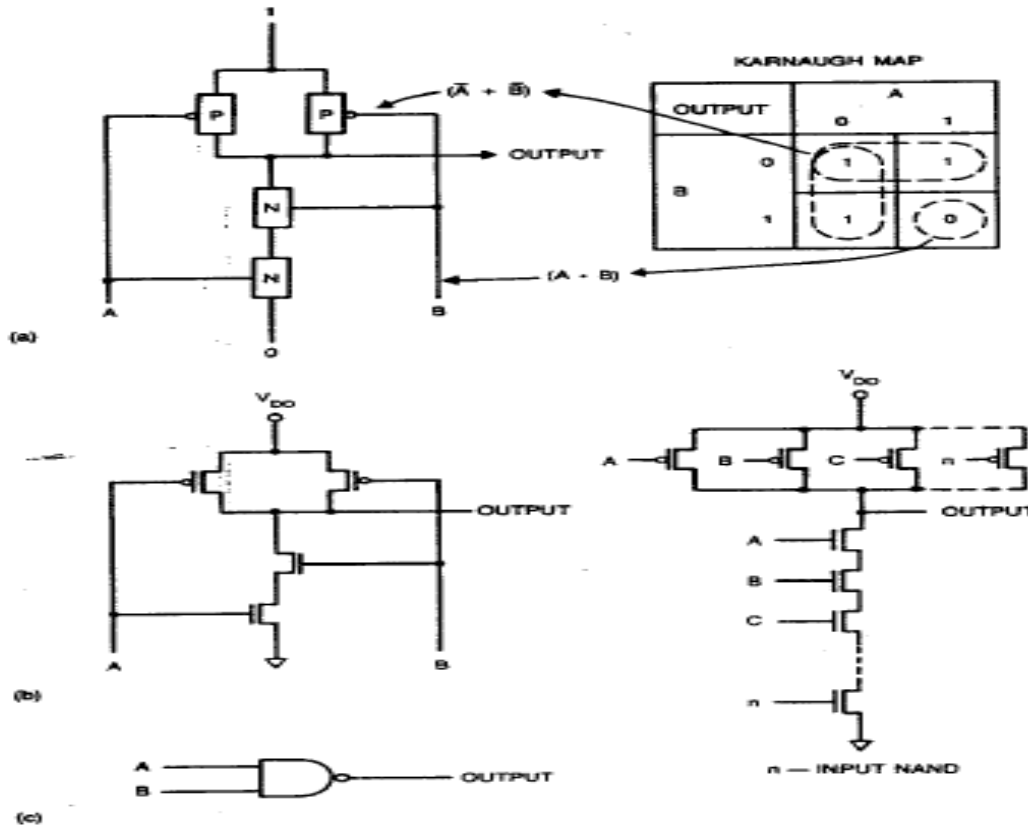


FIGURE 1.6. A CMOS NAND gate

TABLE 1.2. NAND gate truth table

| A INPUT | B INPUT | A N-SWITCH | B N-SWITCH | A P-SWITCH | B P-SWITCH | OUTPUT |
|---------|---------|------------|------------|------------|------------|--------|
| 0       | 0       | OFF        | OFF        | ON         | ON         | 1      |
| 0       | 1       | OFF        | ON         | ON         | OFF        | 1      |
| 1       | 0       | ON         | OFF        | ON         | OFF        | 1      |
| 1       | 1       | ON         | ON         | OFF        | OFF        | 0      |

# CMOS NOR Gate


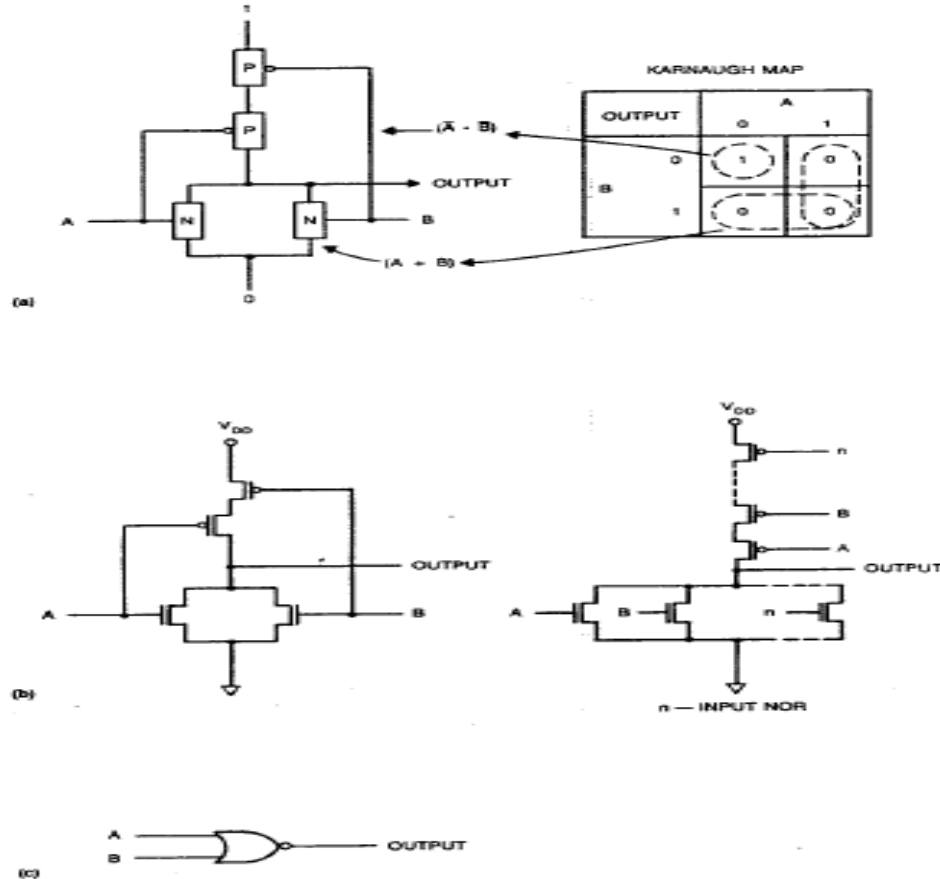


TABLE 1.3. NOR gate truth table

| A INPUT | B INPUT | A N-SWITCH | B N-SWITCH | A P-SWITCH | B P-SWITCH | OUTPUT |
|---------|---------|------------|------------|------------|------------|--------|
| 0       | 0       | OFF        | OFF        | ON         | ON         | 1      |
| 0       | 1       | OFF        | ON         | ON         | OFF        | 0      |
| 1       | 0       | ON         | OFF        | OFF        | ON         | 0      |
| 1       | 1       | ON         | ON         | OFF        | OFF        | 0      |

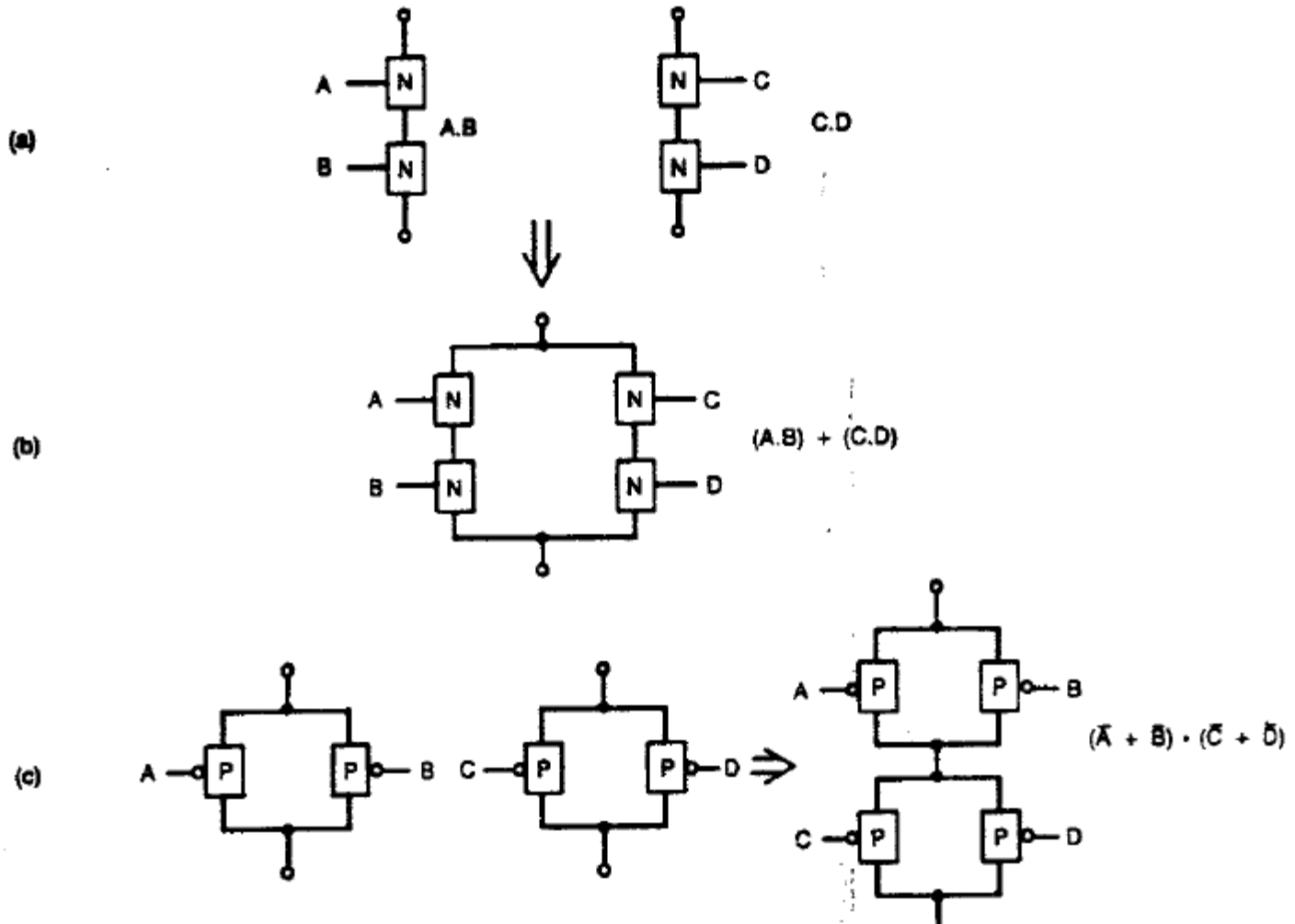
# Compound Gates- $F = \overline{((A.B) + (C.D))}$






# Contd..

(d)

 

$$F = \overline{((A \cdot B) + (C \cdot D))}$$

(e)

 

**FIGURE 1.8.** Construction of function  $F = \overline{((A \cdot B) + (C \cdot D))}$

# 2 to 1 Multiplexer


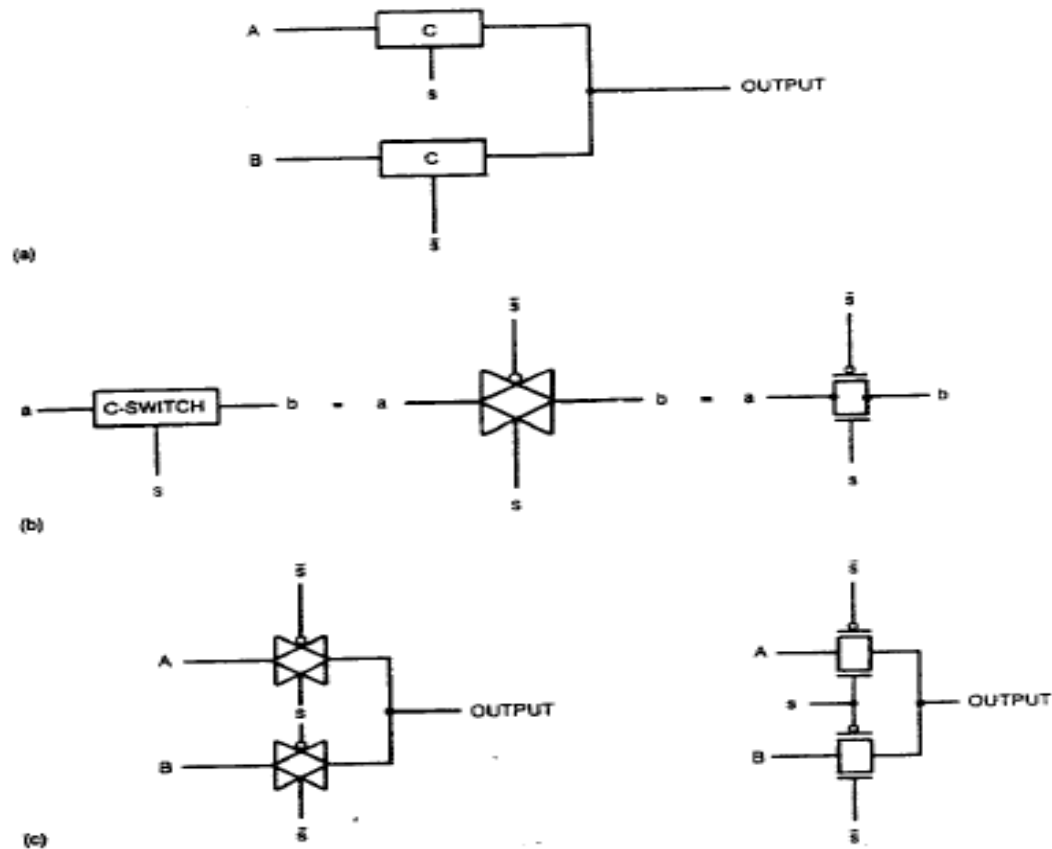
 
 


FIGURE 1.10. A CMOS 2-input multiplexer

TABLE 1.4. Two input multiplexer truth table

| A | B | S | $\bar{S}$ | OUTPUT |
|---|---|---|-----------|--------|
| X | 0 | 0 | 1         | 0(B)   |
| X | 1 | 0 | 1         | 1(B)   |
| 0 | X | 1 | 0         | 0(A)   |
| 1 | X | 1 | 0         | 1(A)   |

# CMOS Flipflop

 

When  $LD = '1'$ ,  $\bar{Q}$  is set to  $\bar{D}$  and  $Q$  is set to  $D$  (Fig. 1.11b). When  $LD$  is switched to '0', a feedback path around the inverter pair is established (Fig. 1.11c). This causes the current state of  $Q$  to be stored. While  $LD = '0'$  the input  $D$  is ignored.

# Alternate circuit Representation- Behavioral Representation

- $F = \overline{(A+B+C)}.D$
- Sum = a + b
- If (LD=1)
- Then
- Q=D;

# Alternate circuit Representation- structural Representation-inverter

```
Part  inv  (in)-> out
      Nfet out  in  vss
      Pfet out  in  vdd
End
```

```
Transistor-type  drain-conn  gate-conn  source-conn
      Nfet          out        in        vss
```


Thus the first statement describes an n-transistor with drain = out, gate = in, source = vss. The second statement describes a p-transistor with drain = out, gate = in, source = vdd.

# 2 input NAND gate-Behavioral Description

The description for a 2-input NAND gate would be

```
Part nand2 (a,b) -> out
Signal il
  Nfet il a vss
  Nfet out b il
  Pfet out a vdd
  Pfet out b vdd
End
```


$$\text{out} = \neg(a \& b)$$

 

-al
 
# 2 input NAND gate-Structural Description





```
Part nand2 (a,b) -> out
Signal il
  Mfet il a vss
  Mfet out b il
  Pfet out a vdd size = 2
  Pfet out b vdd size = 2
  Capacitance il 50
  Capacitance a 100
  Capacitance b 100
  Capacitance out 200
End
```


    
# Flipflop



```

Part flipflop (in, ld, ldbar, q, qbar)
Signal a
  tg (in, ld, ldbar) -> a
  inv (a) -> qbar
  inv (qbar) -> q
  tg (q, ldbar, ld) -> a
End
  
```







# Physical Representation-NMOS & PMOS

  

# Physical Representation-Inverter

 
 
# Physical Representation-Transmission Gate



# CMOS V/S NMOS

## •Comparison:

| Feature              | CMOS (Complementary)                       | NMOS (Single Type)                                 |
|----------------------|--|--|
| Power Consumption    | Low (except during switching)              | Higher (due to static current flow)                |
| Speed                | High (due to low capacitance)              | High (but can be slower in certain configurations) |
| Logic Implementation | More flexible, used in large-scale designs | Simple but less efficient                          |
| Drive Current        | Better (due to use of both PMOS and NMOS)  | Limited (only one type of transistor)              |